

# Hardware Implementation

## Lecture B17



Lecture notes section B17

2002-10-17

CSEI 303 Part B lecture notes

1

## Last time

- Analysis of translation
- Writing efficient C

2002-10-17

CSEI 303 Part B lecture notes

2

## In this lecture

- Gates
- Combinatorial logic
  - adder
  - ALU
- Sequential logic
  - flip-flop
  - memory
- CPU
  - fetch-execute cycle

2002-10-17

CSEI 303 Part B lecture notes

3

## How to make a computer

- Computers are electronic equipment
  - contain many connected electronic components
    - memory
    - Central Processing Unit (CPU)
    - specialized devices (network, video, etc.)
  - components largely made of circuits containing wires and gates

2002-10-17

CSEI 303 Part B lecture notes

4

## Gates


- Tiny electronic switches
  - made of transistors
  - implement Boolean logic
    - 0/1  $\Leftrightarrow$  low/high voltage
    - digital
  - for given inputs, produce known output
    - according to truth table
  - represented in circuit diagrams by symbols

2002-10-17

CSEI 303 Part B lecture notes

5

## Gates

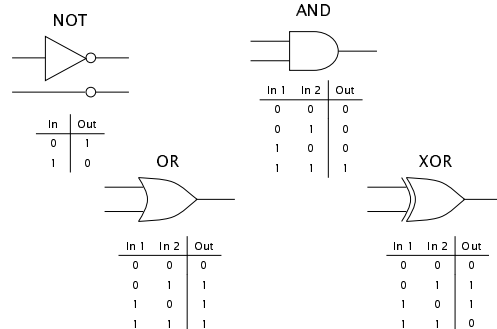

2002-10-17

CSEI 303 Part B lecture notes

6

## Combinatorial logic

- What about more complex truth tables?
- Made by combining many gates together
  - wires connect inputs and outputs
  - each wire can carry only one bit, 0 or 1

2002-10-17

CSEI 303 Part B lecture notes

7

## Combinatorial logic

- Circuits made from collections of gates
  - outputs depend only on inputs
    - not on prior state
  - characterized by truth table
  - comparable to Boolean expression


2002-10-17

CSEI 303 Part B lecture notes

8

## Combinatorial logic

$$X = (A \& \sim B) | (B \& C)$$

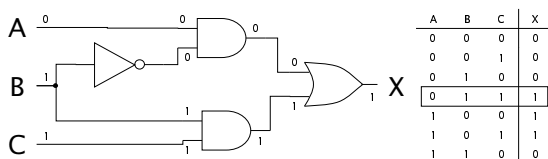

| A | B | C | X |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

All three of these are equivalent; each can be converted to the other two.

2002-10-17

CSEI 303 Part B lecture notes

9

## Combinatorial logic

- Many parts of a computer are constructed of combinatorial logic
  - adder circuit
    - performs addition
  - arithmetic logic unit (ALU)
    - performs many kinds of arithmetic
    - contains adder circuit
  - multiplexer and decoder
    - direct bit traffic between components

2002-10-17

CSEI 303 Part B lecture notes

10

## Adder

- A combinatorial circuit that adds binary values
  - according to this truth table

| In 1 | In 2 | Sum | Carry |
|------|------|-----|-------|
| 0    | 0    | 0   | 0     |
| 0    | 1    | 1   | 0     |
| 1    | 0    | 1   | 0     |
| 1    | 1    | 0   | 1     |

Sum is equivalent to XOR


Carry is equivalent to AND

2002-10-17

CSEI 303 Part B lecture notes

11

## Adder

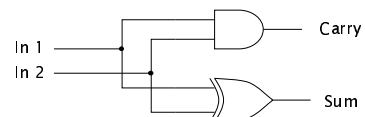

This circuit can add two binary digits and is called a half-adder

2002-10-17

CSEI 303 Part B lecture notes

12

## Adder

Why "half-adder" . . . ?

|   |   |   |   |
|---|---|---|---|
|   |   | 1 |   |
|   | 1 | 5 | 3 |
| + | 4 | 3 | 8 |
|   |   | 9 | 1 |

. . . because to add multi-digit numbers each column requires two additions

2002-10-17 CSEI 303 Part B lecture notes 13

## Full adder

This circuit is called a full adder and can add three binary digits

This OR gate combines the carries from the two half-adders

2002-10-17 CSEI 303 Part B lecture notes 14

## Ripple-carry adder

2002-10-17 CSEI 303 Part B lecture notes 15

## Ripple-carry adder

0101 + 0110 = 1011

2002-10-17 CSEI 303 Part B lecture notes 16

## Ripple-carry adder

- So named because gate results (including carries) propagate ("ripple") from LSB to MSB
  - right to left
  - corresponds to how humans add numbers with pen and paper
- More sophisticated, faster, adder circuits exist
  - see CSE3304

2002-10-17 CSEI 303 Part B lecture notes 17

## Adder

Adders (and other arithmetic circuits) are usually drawn like this in block diagrams

collections of parallel, related wires like this are known as buses; they carry multi-bit values between components

2002-10-17 CSEI 303 Part B lecture notes 18

## Arithmetic


- Computers need to do more than just addition
  - arithmetic:  $+$   $-$   $*$   $/$   $\%$
  - logic:  $\&$   $|$   $\sim$   $\ll$   $\gg$
- Need a circuit that can select operation to perform

2002-10-17

CSE1 303 Part B lecture notes

19

## Arithmetic Logic Unit (ALU)

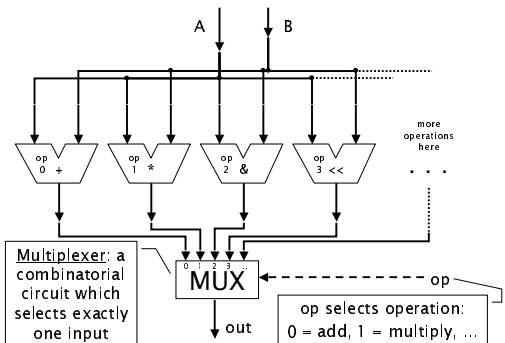


2002-10-17

CSE1 303 Part B lecture notes

20

## Arithmetic Logic Unit (ALU)

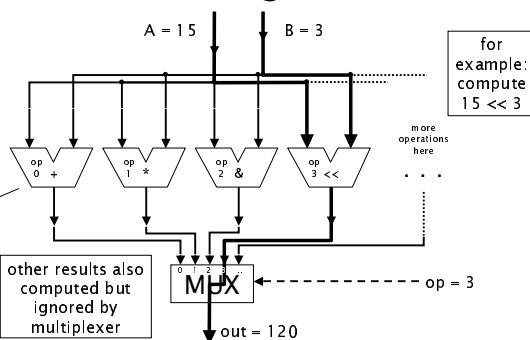

2002-10-17

CSE1 303 Part B lecture notes

21

## Memory

- Computers need memory for storage
- Different kinds of memory distinguished by speed, size, cost and proximity to CPU
  - main memory
    - slowish, huge, cheap, far from CPU
    - typical size  $10^9$  bits
  - cache
    - fast, medium-sized, expensive, near to CPU
    - typical size  $10^6$  bits
  - registers
    - extremely fast, tiny, very expensive, located on CPU
    - in MIPS  $32 \times 32 = 1024$  bits

2002-10-17

CSE1 303 Part B lecture notes

22

## Memory

- The smallest piece of memory is a single binary digit (bit)
  - can hold 0 or 1 only
- A one-bit memory is called a flip-flop or latch
  - because its value can flip and flop between 0 and 1
  - because it can latch onto a value and store it

2002-10-17

CSE1 303 Part B lecture notes

23

## Flip-flop

- Flip-flop needs two operation modes
  - write: store (memorize) a value
  - read: load (recall) a previously stored value
- Also need
  - data in
    - for telling flip-flop what value to store (0 or 1)
    - used only when writing
  - data out
    - for finding out what value flip-flop currently contains (0 or 1)
    - used only when reading

2002-10-17

CSE1 303 Part B lecture notes

24

## Flip-flop


- Flip-flop can be implemented with gates
- Not combinatorial logic
  - because current output may depend on previous state
- Example of sequential logic
  - current output depends on inputs and prior output

2002-10-17

CSE1 303 Part B lecture notes

25

## Flip-flop

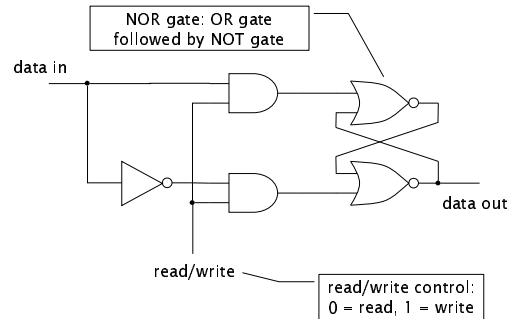


2002-10-17

CSE1 303 Part B lecture notes

26

## Flip-flop: writing

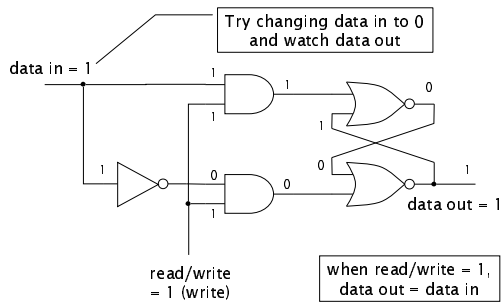


2002-10-17

CSE1 303 Part B lecture notes

27

## Flip-flop: reading

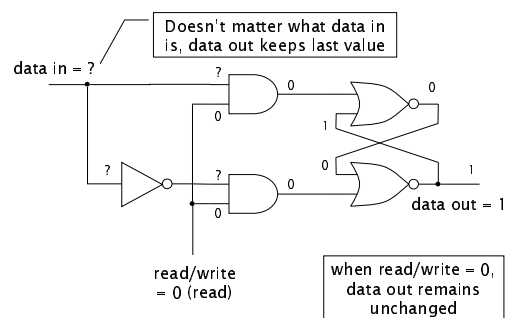


2002-10-17

CSE1 303 Part B lecture notes

28
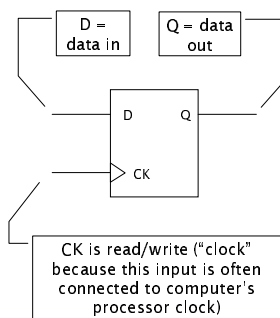
## Flip-flop

Flip-flops are often drawn like this in block diagrams



2002-10-17

CSE1 303 Part B lecture notes

29




## Memory

- Memory can store many bits independently
  - many flip-flops
- Need to identify which bit (flip-flop) to read or write
- Give each flip-flop a unique number (address)

2002-10-17


CSE1 303 Part B lecture notes





30

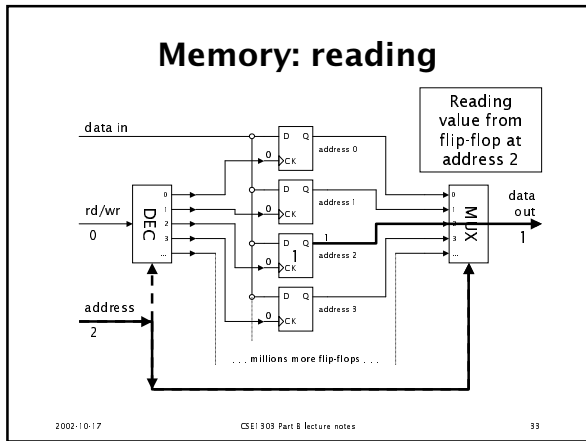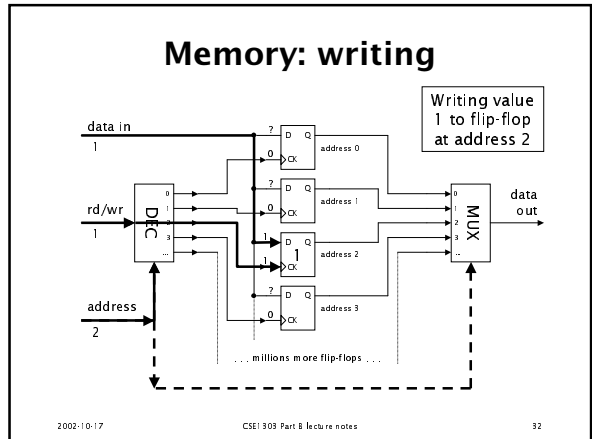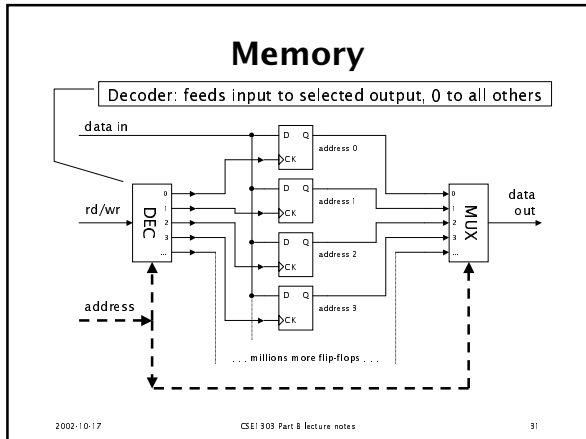

- ### Memory
- Memory usually operates in terms of bytes (8 bits), not single bits
  - Repeat memory circuit eight times
    - connect each memory circuit to one of the eight lanes of the data bus
    - reads and writes occur in parallel for each bit in byte
- 2002-10-17 CSEI 303 Part B lecture notes 34

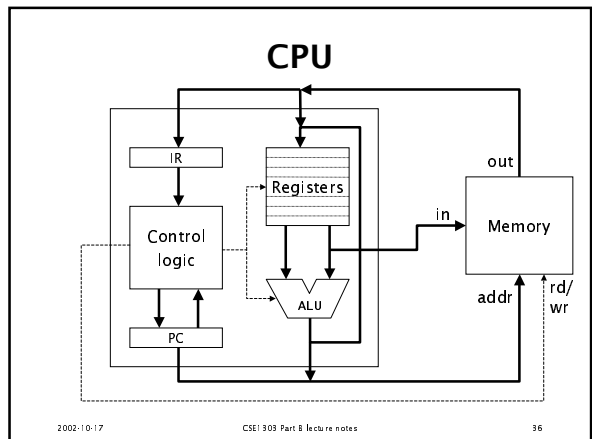- ### Central Processing Unit (CPU)
- Coordinates all computer's components according to program being run
  - Contains
    - registers
    - ALU
    - program counter (PC)
      - address of current instruction
    - instruction register (IR)
      - copy of current instruction
    - control logic
  - Runs programs using fetch-execute cycle
- 2002-10-17 CSEI 303 Part B lecture notes 35



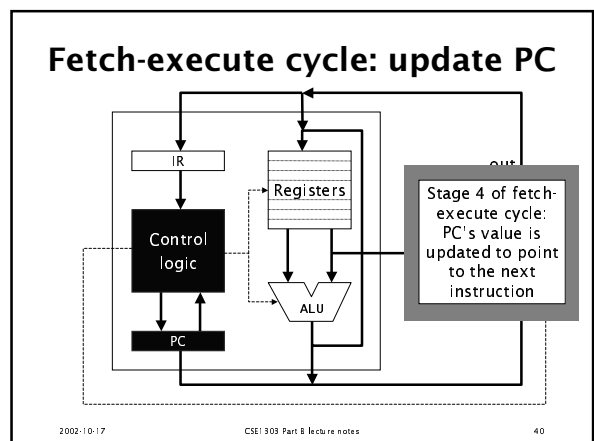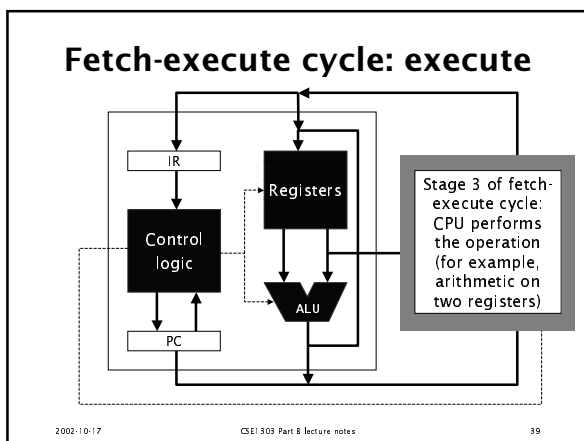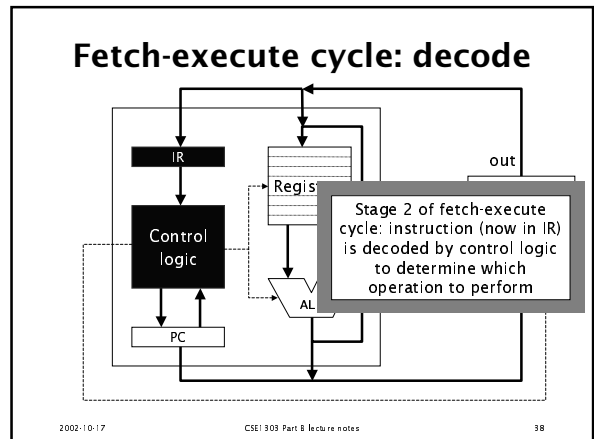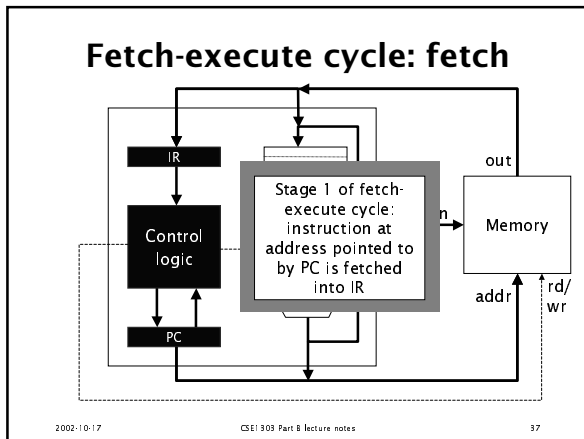

- ### Covered in this lecture
- Gates
  - Combinatorial logic
    - adder
    - ALU
  - Sequential logic
    - flip-flop
    - memory
  - CPU
    - fetch-execute cycle
- 2002-10-17 CSE1309 Part B lecture notes 41

- ### Going further
- Digital logic
    - CSE1101/CSE1308/CSE2306
  - Implementing computers
    - CSE1102
- 2002-10-17 CSE1309 Part B lecture notes 42

## Next time

- Revision

2002-10-17

CSEI 309 Part 8 lecture notes

43

## Copyright

Copyright © 2002 Deborah Pickett.  
No part of this presentation may be  
duplicated without permission from  
the author.

2002-10-17

CSEI 309 Part 8 lecture notes

44